

**Vedic Multiplier** is a key tool in rapidly growing technology especially in the immense domain of image processing, Digital Signal Processing, real-time signal. Multipliers are important block in digital systems and play a critical role in digital designs.

### **Advantages**

1. consumes 66% less area.
2. 76.1% less power.
3. 60% less delay

**The Vedic multiplier** is a technique used in ancient Indian mathematics, specifically within Vedic mathematics, for multiplying two numbers. It involves breaking down the numbers, applying mental calculation using specific sutras, and combining the results to obtain the final product.

How it is different from normal multiplier?

VEDIC multiplier is a good alternative to the other fast multiplicative algorithms. VEDIC multipliers reduces hardware as well as the delay compared to other algorithms.

### **1. Methodology:-**

The Vedic multiplier employs specific sutras from Vedic mathematics to simplify and speed up the multiplication process. It focus on mental calculations and breaking down the numbers into smaller components, whereas the normal multiplier follows a step by step algorithm approach.

### **2. Speed and Efficiency:-**

The Vedic multiplier is known for its speed and efficiency in mental calculations. It allows for quicker computations compared to the conventional long multiplication method, particularly for certain types of numbers.

### **3. Flexibility:-**

The Vedic multiplier offers more flexibility in terms of the numbers it can handle. It can be applied to various types of numbers, including large numbers, decimals, and fractions, making it a versatile technique.

### **4. Educational Focus:-**

The Vedic multiplier is often taught as part of vedic mathematics courses or mental calculation techniques. It aims to enhance mathematical skills, mental ability, and overall number sense, while the normal multiplier is typically taught as a standard multiplication algorithm in traditional mathematics education.

## 4 Bit Vedic Multiplier

				$A_3$	$A_2$	$A_1$	$A_0$
				$B_3$	$B_2$	$B_1$	$B_0$
			$A_3B_0$	$A_2B_0$	$A_1B_0$	$A_0B_0$	
		$A_3B_1$	$A_2B_1$	$A_1B_1$	$A_0B_1$		X
	$A_3B_2$	$A_2B_2$	$A_1B_2$	$A_0B_2$		X	
	$A_3B_3$	$A_2B_3$	$A_1B_3$	$A_0B_3$			

---


$P_7$	$P_6$	$P_5$	$P_4$	$P_3$	$P_2$	$P_1$	$P_0$
-------	-------	-------	-------	-------	-------	-------	-------

---


$P_0 = A_0B_0$   
 $P_1 = A_1B_0 + A_0B_1$   
 $P_2 = A_2B_0 + A_1B_1 + A_0B_2$   
 $P_3 = A_3B_0 + A_2B_1 + A_1B_2 + A_0B_3$   
 $P_4 = A_3B_1 + A_2B_2 + A_1B_3$   
 $P_5 = A_3B_2 + A_2B_3$   
 $P_6 = A_3B_3$  ,  $P_7 = \text{carry from } P_6$

$$A_0 B_0 \xrightarrow{w_1} P_0$$


$$P_1 = A_1 B_0 + A_0 B_1$$

 


$$P_2 = A_2 B_0 + A_1 B_1 + A_0 B_2$$

 

 
$$P_3 = A_3 B_0 + A_2 B_1 + A_1 B_2 + A_0 B_3$$




$$P_4 = A_3 B_1 + A_2 B_2 + A_1 B_3$$

 

 


$$P_5 = A_3 B_2 + A_2 B_3$$

 

$$P_6 = A_3 B_3$$



## Code for 4 Bit

```
12
13  module fourbitmultiplier(p,a,b);
14 input [3:0]a;
15 input [3:0]b;
16 output [7:0]p;
17 wire [7:0]p;
18 wire c1,c2,c3,c4,c5,k1,k2,k3,k4,k5,k6,s1,s2,s3,s4,s5,s6;
19 wire w1,w2,w3,w4,w5,w6,w7,w8,w9,w10,w11,w12,w13,w14,w15,w16;
20  ☐ and X1(p[0],a[0],b[0]);
21
22 ☐ and X2(w2,a[1],b[0]);
23 ☐ and X3(w3,a[0],b[1]);
24 halfadder HA1(p[1],c1,w2,w3);
25
26 ☐ and A4(w4,a[2],b[0]);
27 ☐ and A5(w5,a[1],b[1]);
28 ☐ and A6(w6,a[0],b[2]);
29 fulladder FA1(s1,k1,w4,w5,w6);
30 halfadder HA2(p[2],c2,s1,c1);
31
32 ☐ and A7(w7,a[3],b[0]);
33 ☐ and A8(w8,a[2],b[1]);
34 ☐ and A9(w9,a[1],b[2]);
35 fulladder FA2(s2,k2,w7,w8,w9);
36 ☐ and A10(w10,a[0],b[3]);
37 halfadder HA3(s3,k3,s2,w10);
38 fulladder FA3(p[3],c3,s3,k1,c2);
39
40 ☐ and A11(w11,a[3],b[1]);
41 ☐ and A12(w12,a[2],b[2]);
42 ☐ and A13(w13,a[1],b[3]);
43 fulladder FA4(s4,k4,w11,w12,w13);
44 halfadder HA4(s5,k5,s4,k2);
45 fulladder FA5(p[4],c4,s5,k3,c3);
46
47 ☐ and A14(w14,a[3],b[2]);
48 ☐ and A15(w15,a[2],b[3]);
49 fulladder FA6(s6,k6,w14,w15,k4);
50 fulladder FA7(p[5],c5,s6,k5,c4);
51
52 ☐ and A16(w16,a[3],b[3]);
53 fulladder FA8(p[6],p[7],w16,k6,c5);
54  endmodule
55
```


```

51 |
52 | ○ and A16(w16,a[3],b[3]);
53 | fulladder FA8(p[6],p[7],w16,k6,c5);
54 | ⊞ endmodule
55 |
56 |
57 | ⊞ module halfadder(sum,carry,x,y);
58 | input x,y;
59 | output sum,carry;
60 | wire sum,carry;
61 | ○ xor X1(sum,x,y);
62 | ○ and Y1(carry,x,y);
63 | ⊞ endmodule
64 |
65 | ⊞ module fulladder(sum1,carry1,x1,y1,cin);
66 | input x1,y1,cin;
67 | output sum1,carry1;
68 | wire k1,k2,k3;
69 | ○ xor X1(k1,x1,y1);
70 | ○ xor X2(sum1,cin,k1);
71 | ○ and X3(k2,cin,k1);
72 | ○ and X4(k3,x1,y1);
73 | ○ or X5(carry1,k3,k2);
74 | ⊞ endmodule
-- |

```



**Schematic Diagram**

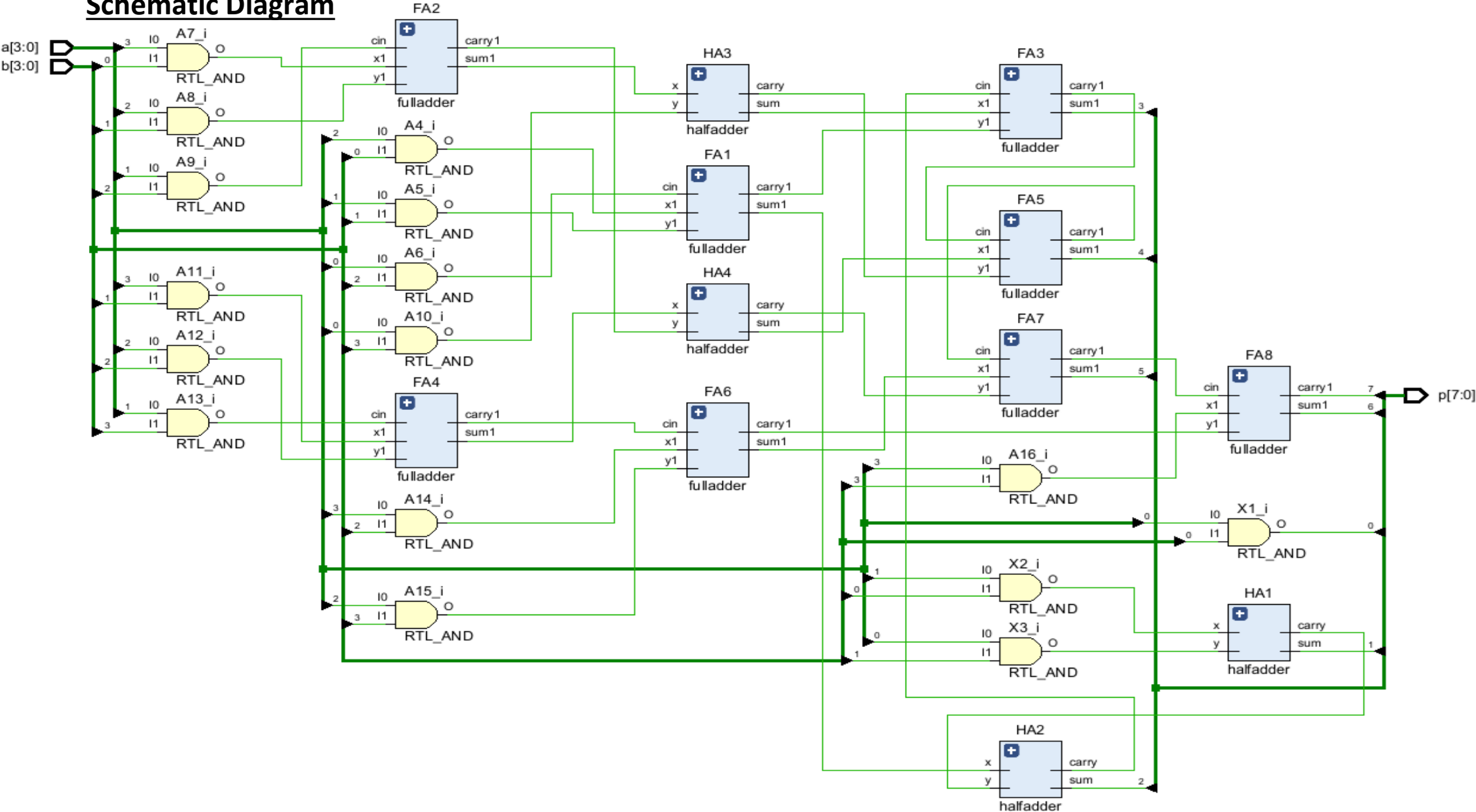

## Test Bench

```

module fourbitmultiplier_tb();
  wire [0:7]p;
  reg [0:3]a,b;
  fourbitmultiplier Multiplier4_bit(p,a,b);
  initial
  begin
    a=4'b1110; b=4'b0111;
    #5 a=4'b1000; b=4'b1000;
    #5 a=4'b1111; b=4'b1111;
    #5 a=4'b1110; b=4'b1110;
    #5 a=4'b0111; b=4'b1101;
    #5 a=4'b1011; b=4'b1101;
  end
  initial $monitor($time,"a= %b,b= %b,p= %d", a, b, p);
  initial #100 $stop;
endmodule

```


# run 1000ns

## Result


0a= 1110,b= 0111,p= 98  
 5a= 1000,b= 1000,p= 64  
 10a= 1111,b= 1111,p= 225  
 15a= 1110,b= 1110,p= 196  
 20a= 0111,b= 1101,p= 91  
 25a= 1011,b= 1101,p= 143

Results are in Decimal number.


## Wavefor

 



 

 $A = 4'b1101$  i.e 13 and  $B = 4'b1011$  i.e. 11  
Output =  $13 * 11 = 143$  ( $8'b10001111$ )



$A = 4'b1101$  i.e. 13 and  $B = 4'b0111$  i.e. 7  
Output =  $13 * 7 = 91$  ( $8'b01011011$ )



$A = 4'b1000$  i.e. 8 and  $B = 4'b1000$  i.e. 8  
Output =  $8 * 8 = 64$  ( $8'b01000000$ )




$A = 4'b1110$  i.e. 14 and  $B = 4'b0111$  i.e. 7  
Output =  $14 * 7 = 98$  ( $8'b01100010$ )




## 8 Bit Vedic Multiplier

																$y_7$	$y_6$	$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$
																$x_7$	$x_6$	$x_5$	$x_4$	$x_3$	$x_2$	$x_1$	$x_0$
																$p_{70}$	$p_{60}$	$p_{50}$	$p_{40}$	$p_{30}$	$p_{20}$	$p_{10}$	$p_{00}$
																$p_{71}$	$p_{61}$	$p_{51}$	$p_{41}$	$p_{31}$	$p_{21}$	$p_{11}$	$p_{01}$
																$p_{72}$	$p_{62}$	$p_{52}$	$p_{42}$	$p_{32}$	$p_{22}$	$p_{12}$	$p_{02}$
																$p_{73}$	$p_{63}$	$p_{53}$	$p_{43}$	$p_{33}$	$p_{23}$	$p_{13}$	$p_{03}$
																$p_{74}$	$p_{64}$	$p_{54}$	$p_{44}$	$p_{34}$	$p_{24}$	$p_{14}$	$p_{04}$
																$p_{75}$	$p_{65}$	$p_{55}$	$p_{45}$	$p_{35}$	$p_{25}$	$p_{15}$	$p_{05}$
																$p_{76}$	$p_{66}$	$p_{56}$	$p_{46}$	$p_{36}$	$p_{26}$	$p_{16}$	$p_{06}$
																$p_{77}$	$p_{67}$	$p_{57}$	$p_{47}$	$p_{37}$	$p_{27}$	$p_{17}$	$p_{07}$
$s_{15}$	$s_{14}$	$s_{13}$	$s_{12}$	$s_{11}$	$s_{10}$	$s_9$	$s_8$	$s_7$	$s_6$	$s_5$	$s_4$	$s_3$	$s_2$	$s_1$	$s_0$								


## 2-bit Vedic Multiplier

 

## 4-bit Vedic Multiplier

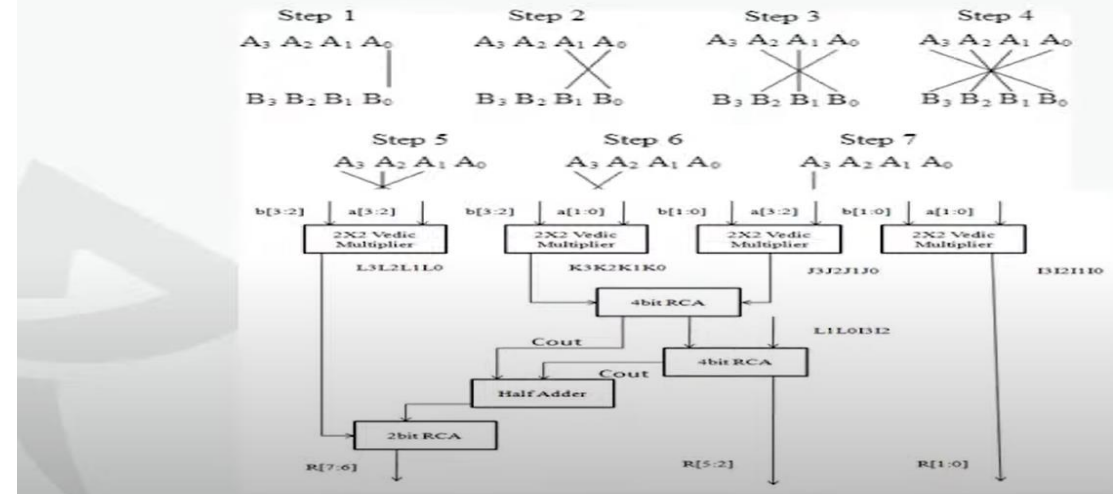

## 8-bit Vedic Multiplier

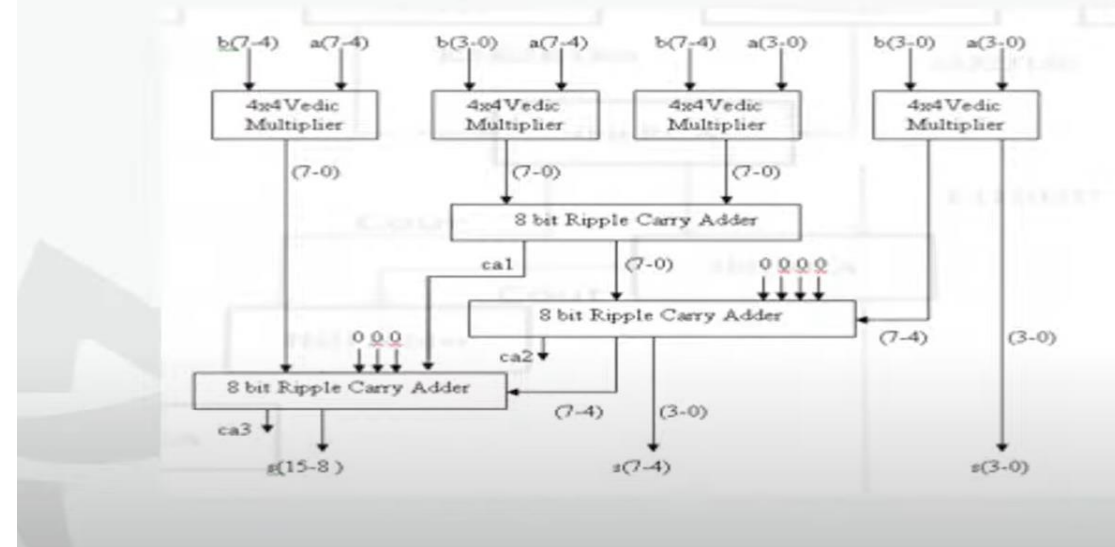

## Code for 8-bit

```
13 module vedic8bit(output [15:0] out,input [7:0] in1,in2);
14     wire[7:0] w1,w2,w3,w4,s1,s2;
15     wire c1,c2,c3;
16     wire [7:0] W1,W2;
17
18     VM4bit VM4BIT_1(w1,in1[3:0],in2[3:0]);
19     VM4bit VM4BIT_2(w2,in1[3:0],in2[7:4]);
20     VM4bit VM4BIT_3(w3,in1[7:4],in2[3:0]);
21     VM4bit VM4BIT_4(w4,in1[7:4],in2[7:4]);
22
23     buf(s1[0],w1[4]);
24     buf(s1[1],w1[5]);
25     buf(s1[2],w1[6]);
26     buf(s1[3],w1[7]);
27     buf(s1[4],0);
28     buf(s1[5],0);
29     buf(s1[6],0);
30     buf(s1[7],0);
31
32
33     ADDER8bit A8_1( c1,W1, w2,w3);
34     ADDER8bit A8_2( c2,W2,W1,s1);
35
36     or o_1(c3,c1,c2);
37
38     buf(s2[0],W2[4]);
39     buf(s2[1],W2[5]);
40     buf(s2[2],W2[6]);
41     buf(s2[3],W2[7]);
42     buf(s2[4],c3);
43     buf(s2[5],0);
44     buf(s2[6],0);
45     buf(s2[7],0);
46
47
48
49
50     assign out[0] = w1[0];
51     assign out[1] = w1[1];
52     assign out[2] = w1[2];
53     assign out[3] = w1[3];
54     assign out[4] = W2[0];
55     assign out[5] = W2[1];
56     assign out[6] = W2[2];
```

```
53     assign out[3] = w1[3];
54     assign out[4] = W2[0];
55     assign out[5] = W2[1];
56     assign out[6] = W2[2];
57     assign out[7] = W2[3];
58
59
60     ADDER8bit A8_3(extra,out [15:8], w4,s2);
61
62
63 endmodule
64
65
66 module VM4bit(output [7:0] out,input [3:0] in1,in2);
67     wire[3:0] w1,w2,w3,w4,s1,s2;
68     wire c1,c2,c3;
69     wire [3:0] W1,W2;
70
71     VM2bit VM2BIT_1(w1,in1[1:0],in2[1:0]);
72     VM2bit VM2BIT_2(w2,in1[1:0],in2[3:2]);
73     VM2bit VM2BIT_3(w3,in1[3:2],in2[1:0]);
74     VM2bit VM2BIT_4(w4,in1[3:2],in2[3:2]);
75
76     buf(s1[0],w1[2]);
77     buf(s1[1],w1[3]);
78     buf(s1[2],0);
79     buf(s1[3],0);
80
81
82     ADDER4bit A4_1( c1,W1, w2,w3);
83     ADDER4bit A4_2( c2,W2,W1,s1);
84
85     or o_1(c3,c1,c2);
86
87     buf(s2[0],W2[2]);
88     buf(s2[1],W2[3]);
89     buf(s2[2],c3);
90     buf(s2[3],0);
91
92
93
94
95     assign out[0] = w1[0];
96     assign out[1] = w1[1];
```

```

94
95     assign out[0] = w1[0];
96     assign out[1] = w1[1];
97     assign out[2] = W2[0];
98     assign out[3] = W2[1];
99
100     ADDER4bit A4_3(extra,out [7:4], w4,s2);
101
102
103 endmodule
104
105 module VM2bit(output [3:0] out, input [1:0] A,B);
106
107     wire [3:0] s;
108
109     and a1(s[0],A[0],B[0]);
110     and a2(s[1],A[0],B[1]);
111     and a3(s[2],A[1],B[0]);
112     and a4(s[3],A[1],B[1]);
113
114     assign out[0] = s[0];
115     halfadder H_1(out[1],C,s[1],s[2]);
116     halfadder H_2(out[2],out[3],s[3],C);
117
118 endmodule
119
120 module ADDER8bit(C,out,A,B );
121     output [7:0] out;
122     output C;
123
124
125
126     input [7:0] A,B;
127     halfadder H_1(out[0],c1,A[0],B[0]);
128     fulladder F_1(out[1],c2,A[1],B[1],c1);
129     fulladder F_2(out[2],c3,A[2],B[2],c2);
130     fulladder F_3(out[3],c4,A[3],B[3],c3);
131     fulladder F_4(out[4],c5,A[4],B[4],c4);
132     fulladder F_5(out[5],c6,A[5],B[5],c5);
133     fulladder F_6(out[6],c7,A[6],B[6],c6);
134     fulladder F_7(out[7],C,A[7],B[7],c7);
135
136 endmodule
137


```

```

136 endmodule
137
138
139 module ADDER4bit(C,out,A,B );
140     output [3:0] out;
141     output C;
142
143
144     input [3:0] A,B;
145     halfadder H_1(out[0],c1,A[0],B[0]);
146     fulladder F_1(out[1],c2,A[1],B[1],c1);
147     fulladder F_2(out[2],c3,A[2],B[2],c2);
148     fulladder F_3(out[3],C,A[3],B[3],c3);
149 endmodule
150
151
152 module halfadder(sum, carry ,A,B);
153     output sum,carry;
154     input A,B;
155
156     assign sum = A^B;
157     assign carry = A&B;
158 endmodule
159
160 module fulladder(sum, carry ,A,B, cin );
161     output sum,carry;
162     input A,B,cin;
163
164
165     assign sum = A^B^cin;
166     assign carry = A&B|B&cin|A&cin;
167
168 endmodule
169

```

## Schematic Diagram

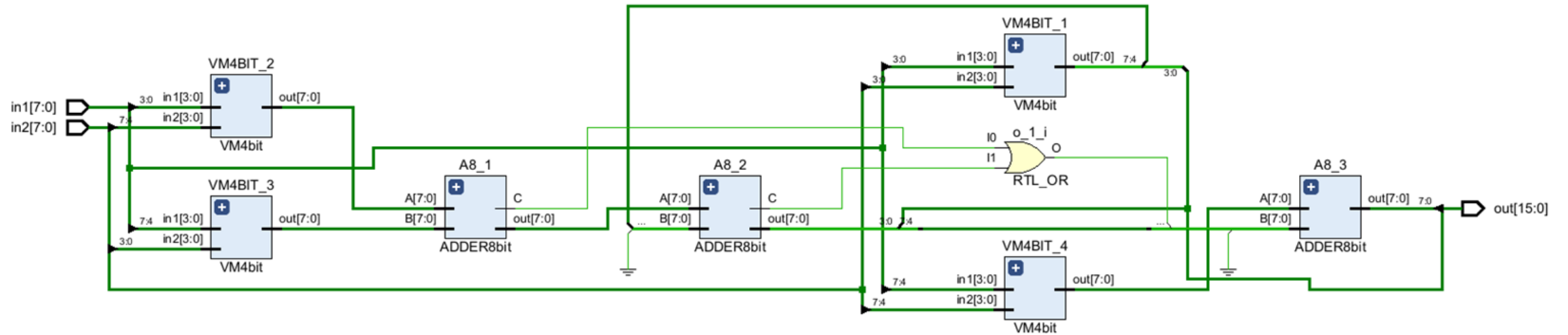

## Test Bench

```
13 |
14 | module vedic8bit_tb();
15 |
16 | wire [0:15]out;
17 | reg [0:7]in1,in2;
18 | vedic8bit Multiplier4_bit(out,in1,in2);
19 | initial
20 | begin
21 |   in1=8'b0001110; in2=8'b00001110;
22 |   #5 in1=8'b10001000; in2=8'b11000000;
23 |   #5 in1=8'b10001110; in2=8'b11000011;
24 | end
25 | initial $monitor($time,"in1= %d,in2= %d,out= %d", in1, in2, out);
26 | initial #100 $stop;
27 | endmodule
```

## Result

```
# run 1000ns
```

```
0in1= 14,in2= 14,out= 196
```

```
5in1= 136,in2= 192,out= 26112
```

```
10in1= 142,in2= 195,out= 27690
```